

Time-Interleaved ADCs, Past and Future

Ken Poulton
Agilent Laboratories

Outline

- ◆ Some History
- ◆ Reasons to Interleave
- ◆ Issues with Interleaving (with examples)
- ◆ Futures

Some History of Interleaving

- ◆ 1980 4-way 100 MSa/s 4 slices/chip CCD (T/H)
Corcoran & Hornak
- ◆ 1980 4-way 4 MSa/s 4 slices/chip CMOS
Hodges & Black
- ◆ 1987 4-way 1 GSa/s 1 slices/chip bipolar + GaAs
Poulton, Corcoran & Hornak
- ◆ 1991 16-way 8 GSa/s 2 slices/chip bipolar
Rush & Byrne
- ◆ 1997 4-way 8 GSa/s 2 slices/chip bipolar
Poulton, Knudsen, Kerley, Kang, Tani, Cornish, VanGrouw
- ◆ 2002 32-way 4 GSa/s 32 slices/chip CMOS
Poulton, Neff, Muto, Liu, Burstein, Heshami
- ◆ 2003 80-way 20 GSa/s 80 slices/chip CMOS
Poulton, Neff, Setterberg, Wuppermann, Kopley, Jewett, Pernillo, Tan, Montijo
- ◆ 2008 16-way 24 GSa/s 64 slices/chip CMOS
Schvan, Bach, Falt, Flemk, Gibbins, Greshishchev, Hamida, Pollex, Sitch, Wang, Wolczanski
- ◆ Trends:
 - Only modest on-chip interleaving until 2002
 - Massively-parallel interleaving introduced in 2002

Why Do Time Interleaving?

- ◆ Highest possible sample rate
 - When you max out the single-ADC sample rate in available technologies, interleaving is the way to further increase sample rate
- ◆ Reduce cost
 - Interleaving has moved multi-GSa/s ADCs from bipolar to CMOS
- ◆ Optimize power
 - CMOS ADCs are generally much more power-efficient
 - Can choose sample rate to optimize power efficiency

Why Not?

- ◆ Interleaving Errors
 - Calibration
- ◆ Extra complexity in HW, possibly SW and system

Issues and Example Solutions

- I'll describe issues for the design of interleaved ADCs, focusing mostly on on-chip interleaving
- I'll describe some example solutions, mostly from our own work


Core ADC Slice

- ◆ Objectives
 - Total power optimization – there is an optimum slice sample rate for a given technology ADC architecture
 - Area
 - Metastable error rate tends to limit sample rate of multi-stage ADCs
 - Calibration – more calibration can allow smaller-area devices with more mismatch

- ◆ Two examples:

Year	1997	2002
Process	25 GHz f_T Bipolar	0.35 μ m CMOS
Sample Rate	4 GSa/s, 7 bits	4 GSa/s, 8 bits
Slices	2x 2 GSa/s	32x 125 MSa/s
Slice Topology	Folded Flash, little calibration	Pipeline w/ stage calibration
Slice Power	3 W	50 mW
Chip Power	13 W	4.5 W


Types of Interleaving Errors

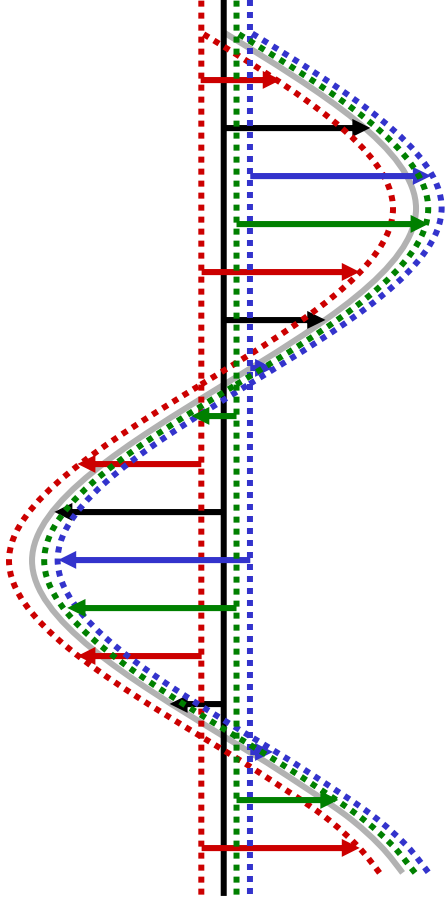

Offset Error


want <0.3% offsets for 8 bits

 - ◆ Errors due to mismatched paths
- ◆ Reconstructed waveform shows distortion.
- ◆ Spurs in the spectrum.



Gain Error

want <0.3% gain matching

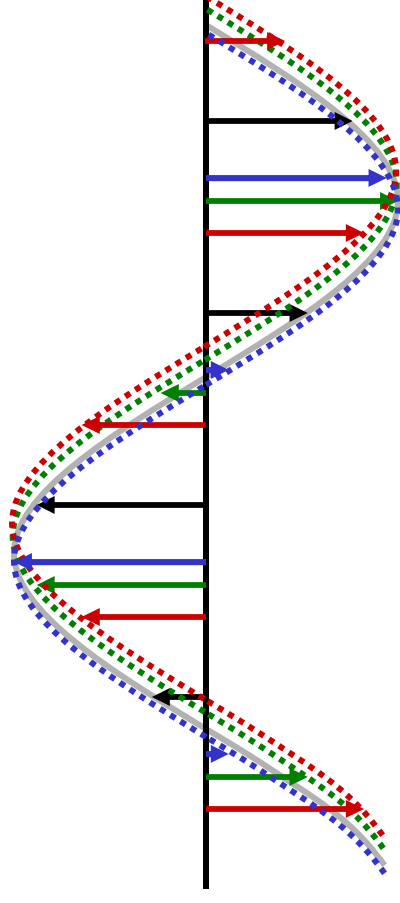

Sampling Instant Error

want <1 ps timing errors
for Fin of 1 GHz


Calibration Choices

- ◆ Calibration Approaches:
 - No Cal: Accurate by design
 - + Simplest in operation
 - Stringent matching requirements -> more area, higher power
 - Risk: any unforeseen mismatch needs a mask turn to fix
 - Analog Cal: Calibrate with adjustable offset, gain and delay DACs or trims
 - + Circuit sizes limited by SNR, not matching => much reduced power
 - + Maximize signal range valid in all slices
 - + Offset and gain adjusts can be low power
 - Delay adjusts add jitter and power
 - Risk: more analog circuits to design
 - Digital Cal: Calibrate with DSP
 - + Circuit sizes limited by SNR, not matching => much reduced power
 - + Fewer analog circuits than analog cal
 - Adds more quantization noise
 - Every adjust adds active data path power
 - +-- Eventually, power of digital corrections will be lower than analog
 - More digital supply noise

More Calibration Choices

- ◆ On-chip vs off-chip calibration (coefficient computation)
 - Off Chip:
 - + lower chip cost
 - + lower design risk
 - much more HW and/or SW complexity for the ADC user
 - On Chip
 - + More generally applicable
 - Higher design cost and risk
- ◆ Foreground calibration vs. Background calibration
 - Foreground
 - + Independent of the input signal
 - ADC user needs to provide cal signals
 - Dead time during calibration
 - Background
 - + Least complexity for the ADC user
 - Places some requirements on the input signal

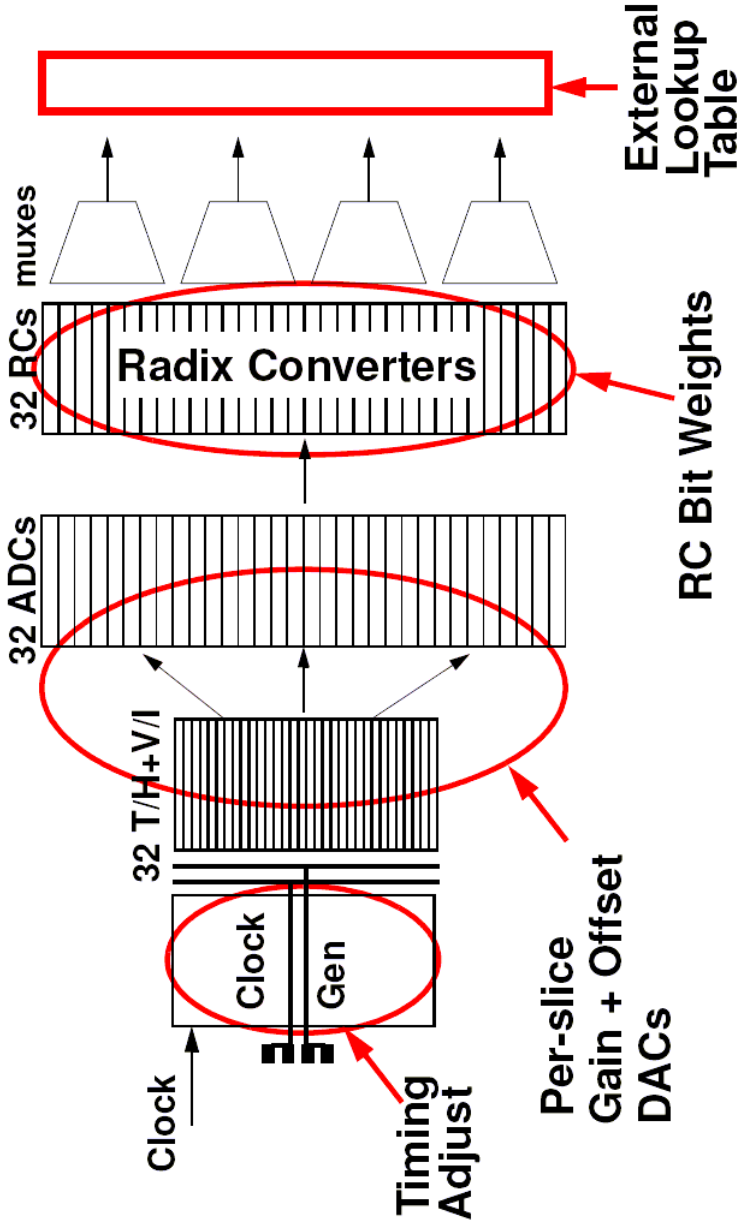
Example of Calibration Choices – 32-way & 80-way CMOS ADCs



- ◆ Oscilloscope application
- ◆ Non-binary-radix pipeline
- ◆ Maximize tolerated offset
- ◆ 0.35, 0.18 um process
- > Foreground calibration
- > Off-chip calibration
- > Digital gain and offset for fine cal
- > Analog cal for coarse gain, offset
- > Adjustable delays for timing cal
- > External lookup for linearity correction

Sample Timing Solutions: Single Samplers

 
- + Relaxes slice clock accuracy requirements
- Requires a full-speed clock and sampler
- Two topologies:



Two-Rank T/H system

+ best T/H BW

Corcoran, et al, ISSCC 1987

 

Two-Switch T/H system

+ lower noise and power


Gupta, et al, ISSCC 2007

Sample Timing Solutions: Interleaved Samplers

- ◆ Interleaved Samplers:
 - + Nothing needs to run at F_S
 - + No critical settling between T/Hs
 - Large C_{IN}
 - Hard to make many equal clock and V_{IN} paths
 - Timing correction usually required

- ◆ Timing Correction Methods:
 - Adjustable delays in clock paths
 - + Corrects the actual sampling instants
 - Drift
 - Delays add jitter and power*Poulton, et al, ISSCC 2002*

  - Delay adjustment by DSP after ADC
 - + Shorter timing paths to drift
 - Timing adjust filters cause gain vs. Fin errors near Nyquist
 - Power and digital noise generation*Jamal, et al, ISSCC 2002*




Accuracy of Clock Generation

- ◆ Single Front-end Sampler
 - One full-accuracy clock (0.1-1 ps rms jitter)
 - N reduced-accuracy clocks (1-10 ps rms jitter and alignment)
 - Second rank requires fairly accurate clocks due to analog settling effects

- ◆ Interleaved front-end samplers
 - N Full-accuracy clocks (0.1-1 ps rms jitter **and** alignment)
 - Generating lots of very-low-jitter clocks can cost a lot of power
 - Simple DLL for N clocks, constant jitter spec:
 - **N stages, with power scaling as N to maintain jitter**
 - **=> Power scales as N²**

- ◆ *For more detail, see: Robert Neff, “Clock Challenges for GHz ADCs”
In the Clock Synthesis Design Forum (F7) on Thursday*

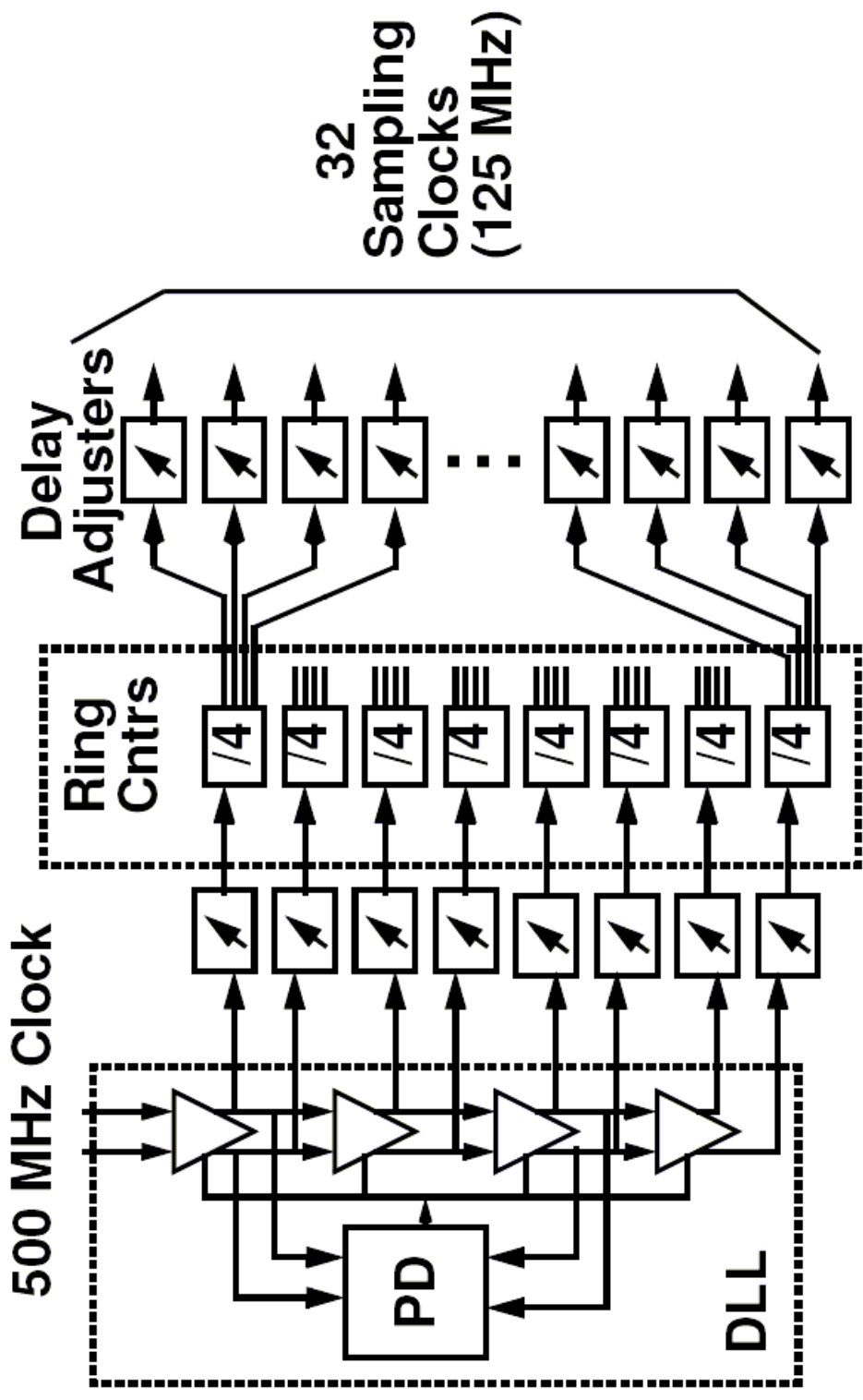Example: Clock Generation for 32-way 4-GSa/s ADC




4 GSa/s: ~ 1 ps thermal jitter

Timing misalignments: before cal: 10 ps rms, after cal: 0.8 ps rms

Clock and Signal Distribution

- ◆ Multiple samplers requires distributing clocks
- ◆ Tradeoff between need for proximity of the samplers and physical size of the ADC slices
- ◆ Both clock and analog signal distribution can take a lot of area and power
- ◆ Example: 80-slice ADC:
 - samplers: 1.9 mm wide
 - ADCs: 9 mm
 - Memory 13 mm


Clock Gen and Samplers

 

Overhead Factors for Interleaved ADCs

- ◆ Power: Even with a power-efficient ADC slice, you can still have a lot of chip power
 - Example: 32-way, 4-GSa/s ADC
 - 32 ADC slices 1.6 W
 - Samplers + clocks 0.9 W
 - Multiplexors and outputs 1.7 W
 - Total 4.2 W
- ◆ Design Overhead:
 - More optimization variables
 - More circuits that interact
 - More clocks
 - V_{IN} and clock distribution
 - Data collection and multiplexing
 - Calibration
 - Optional: Memory and/or DSP

 Historical Data: Relative Design Time vs. Interleave Factor



Where Does All That Data Go?

- ◆ Totally application-dependent
- ◆ Off Chip
 - Wide parallel buses (~ 1 Gb/s per pin) or faster serial ports
 - I/O power can easily be as much as the ADC power
- ◆ On-chip memory
 - Memory power can easily be as much as the ADC power
 - When you need more memory, moving to the next process is a huge redesign for the ADC
- ◆ On-chip DSP
 - A big win if the DSP reduces the amount of data that must be stored or transported off-chip
 - Otherwise, it can be a problem to tie together the ADC process and the DSP process due to different power scaling and development times.

Trends

- ◆ Much more power-efficient core slices
 - Power-Efficiency FOM has dropped by ~10x since 2002
 - Pipelines and SARs dominate
- ◆ More background cal
 - Making the transition from academia to industry
 - Partly enabled by targeting specific apps like communication channels with somewhat-known signals
- ◆ Interleaving is breaking out of “just for scopes”
 - Lots of papers at ISSCC
 - A startup whose major focus is interleaving existing ADCs
 - Massive interleaving for 12-25 Gb/s wireline links
 - Becoming “just another ADC topology”

What is the Future for Interleaved ADCs?

- ◆ When will all ADCs be interleaved?
 - Never!
 - Design complexity
 - Overhead for power and design time
- ◆ When will time-interleaved ADCs become common?
 - It's happening right now

Acknowledgements

- ◆ John Corcoran and Robert Neff of Agilent Labs